



**I Semester B.Sc. Examination, November/December 2010**  
**(Semester Scheme) (O.S) (2004 Onwards)**  
**ELECTRONICS (Paper – I)**  
**Electronic Fundamentals**

Time : 3 Hours

Max. Marks : 60

*Instruction : Answer any five questions from Part – A, four questions from Part – B and five subdivisions from Part – C.*

**PART – A**

Answer any five questions :

**(5×6=30)**

1. a) Explain the construction and working of a carbon composition resistor.  
b) Derive an expression for the energy stored in an inductor.
2. a) With a diagram explain the working of d'A'rsenal movement.  
b) Define an ideal voltage source. When does the practical voltage source behave like stiff voltage source ?
3. a) State and explain voltage divider and current divider theorem.  
b) With a suitable resistive network, explain the steps involved in the analysis of a dc circuit using node voltage method.
4. a) Define the terms, rms value and peak value of an alternating voltage.  
b) An alternating voltage is applied to a circuit having a capacitor C and a resistor R in series. Derive an expression for impedance and current in the circuit.
5. Derive an expression for the impedance of a series RLC circuit using phasor diagram. Draw and explain the impedance curve. What is the condition for the circuit to be at resonance ? Derive an expression for resonant frequency.
6. State and explain :
  - a) Super position theorem
  - b) Reciprocity theorem




7. a) State and explain Kirchoff's current law.  
 b) State and prove maximum power transfer theorem for an ac network.
8. a) Distinguish between Intrinsic semiconductor and Extrinsic semiconductor.  
 b) Discuss the three approximations of a Pn junction diode with relevant equivalent circuit and V-I characteristics.

## PART - B


Answer **any four** questions :

(4×5=20)

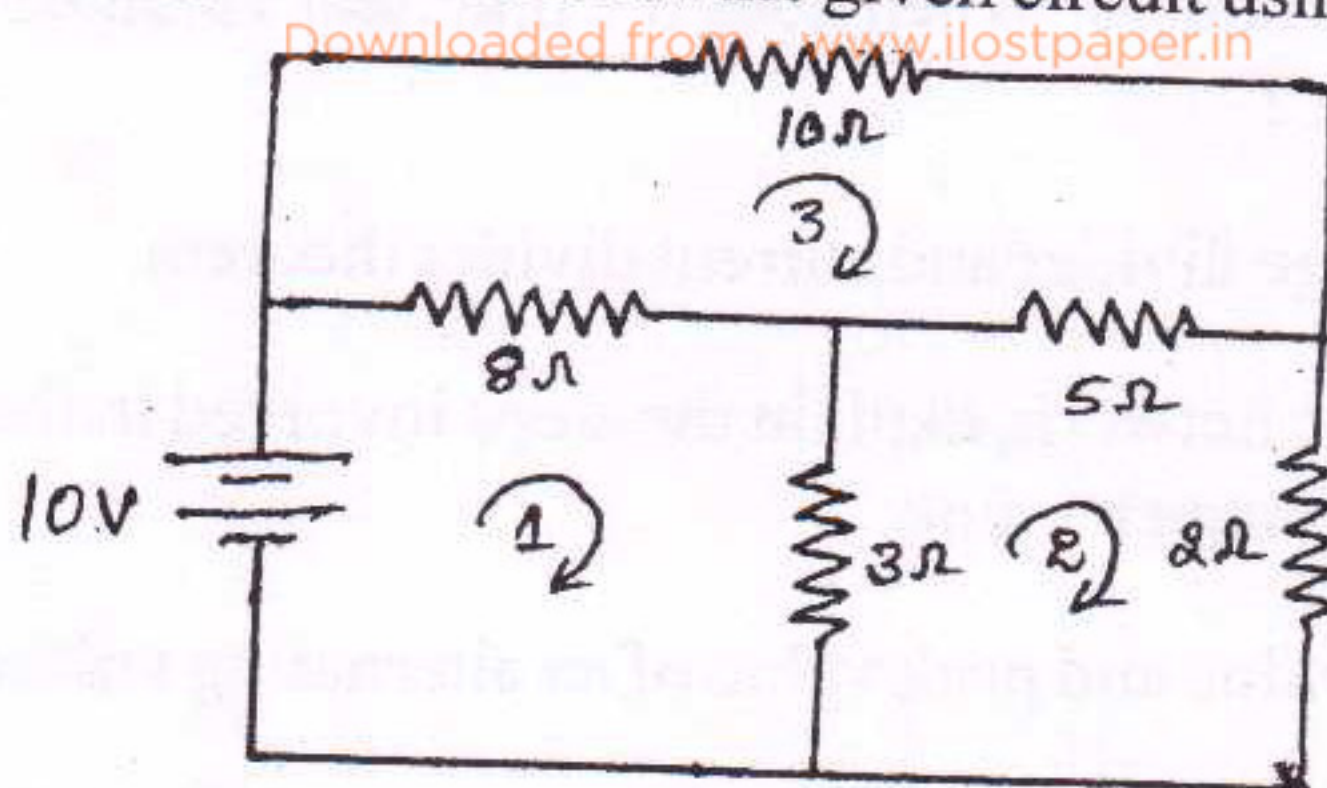9. Two capacitors of capacitance  $10 \mu\text{F}$  and  $20 \mu\text{F}$  are connected in series with a battery of  $100 \text{ V}$ . Calculate :  
 1) Effective capacitance  
 2) Total charge  
 3) The total energy.
10. A dc source of  $100 \text{ V}$ , a resistor of resistance  $1 \text{ K}\Omega$  and inductor of inductance  $5 \text{ H}$  are connected in series, calculate the current after (i)  $5 \text{ ms}$  and (ii)  $15 \text{ ms}$ . Show the variation of current graphically.
11. Find the current through  $3 \Omega$  resistor in the given circuit using mesh current method.



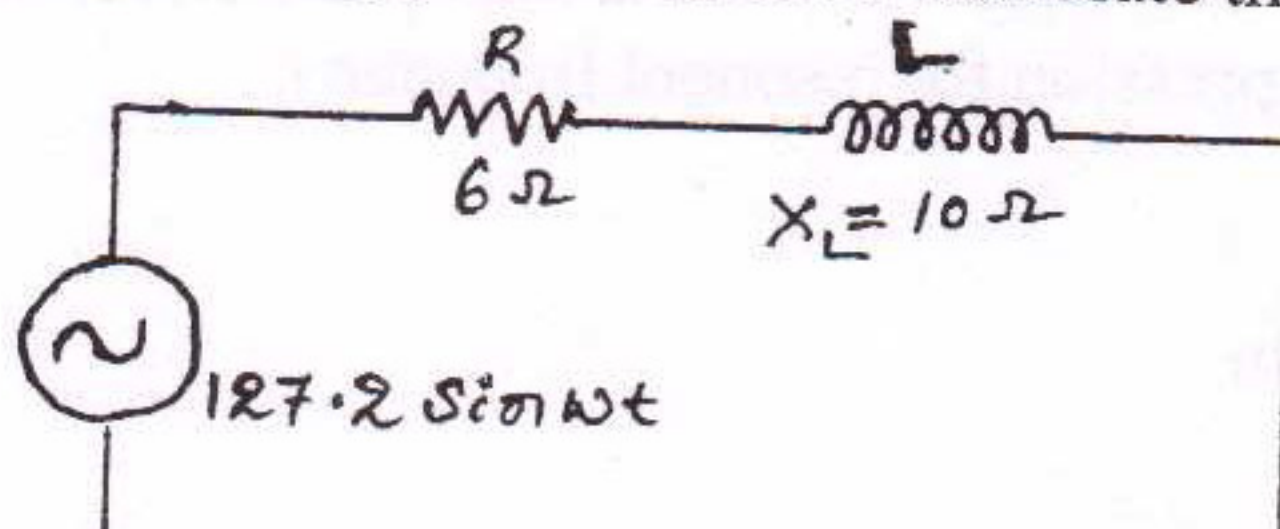
12. Calculate :  
 i) Impedance  
 ii) Voltage drop across R and  
 iii) Voltage drop across L using phasor method. Calculate the power delivered to the circuit.





3. A parallel resonant circuit consists of  $R = 50\Omega$ ,  $L = 50\ \mu\text{H}$  and  $C = 200\ \text{pF}$ . Calculate the
- i) Resonant frequency
  - ii) Impedance at resonance
  - iii) Band width
  - iv) Quality factor.

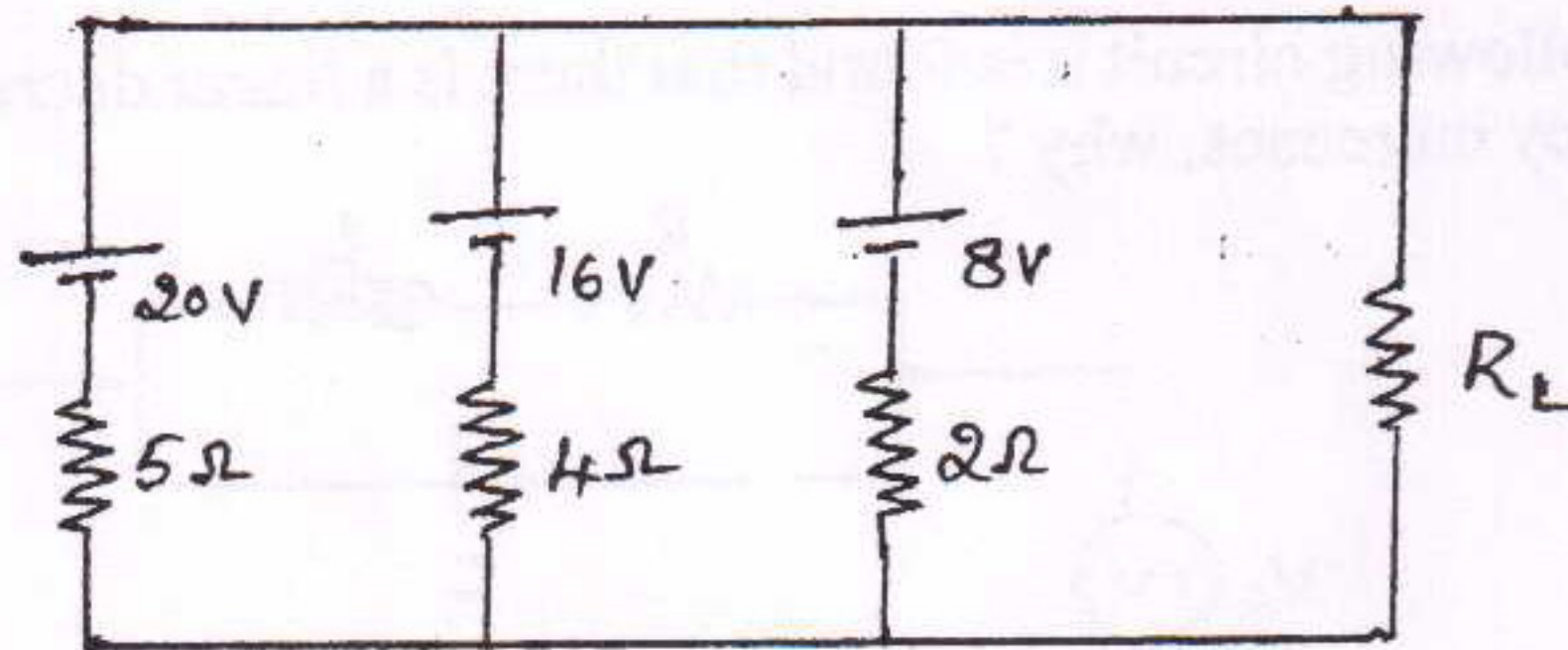14. For the given network find the current through and voltage across the load  $R_L$  using Millman's theorem.




PART - C  
ilost paper


Answer any five subdivisions :

(5x2=10)

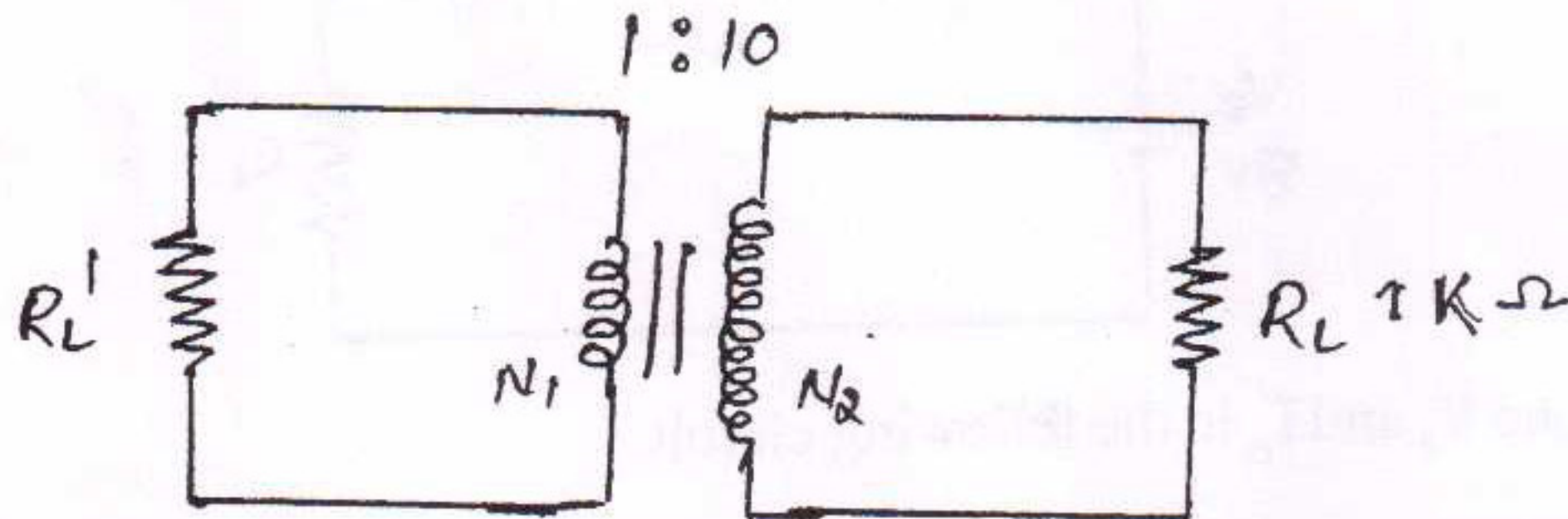
- 15. a) Electrolytic capacitors must be connected with proper polarity. Why ?
- b) What is the value of  $R_i^1$  in the following circuit.



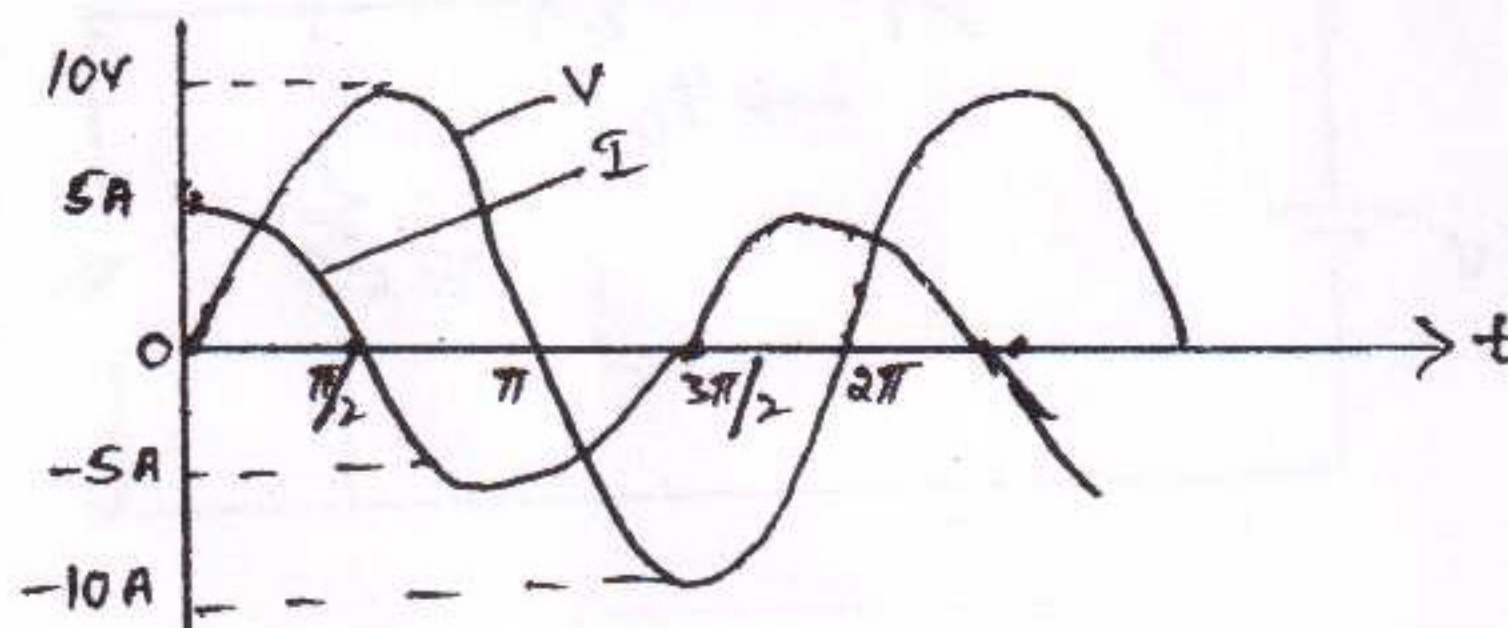
c) The instantaneous voltage  $V$  and resulting current  $i$  through the circuit element are as shown :



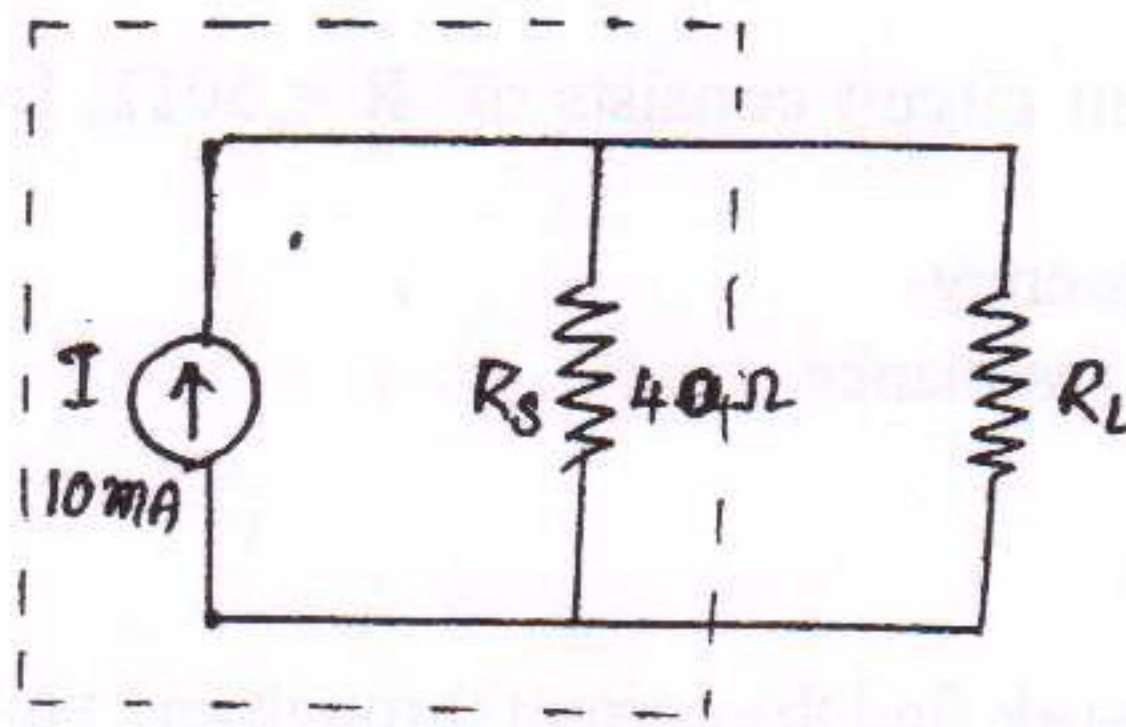
- d) Find the value of  $R_L$  necessary to transfer maximum power to  $R_L$  and calculate the power delivered to  $R_L$ .



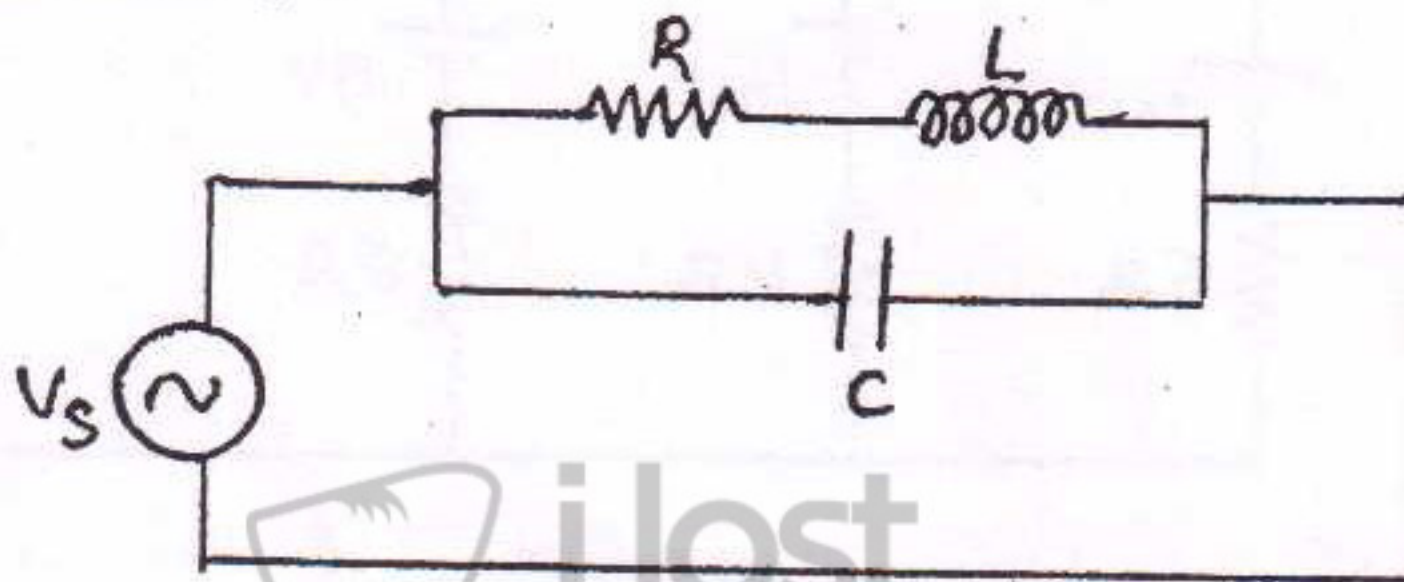- e) In the following circuit it is found that there is a linear decrease in the current as frequency increases, why?



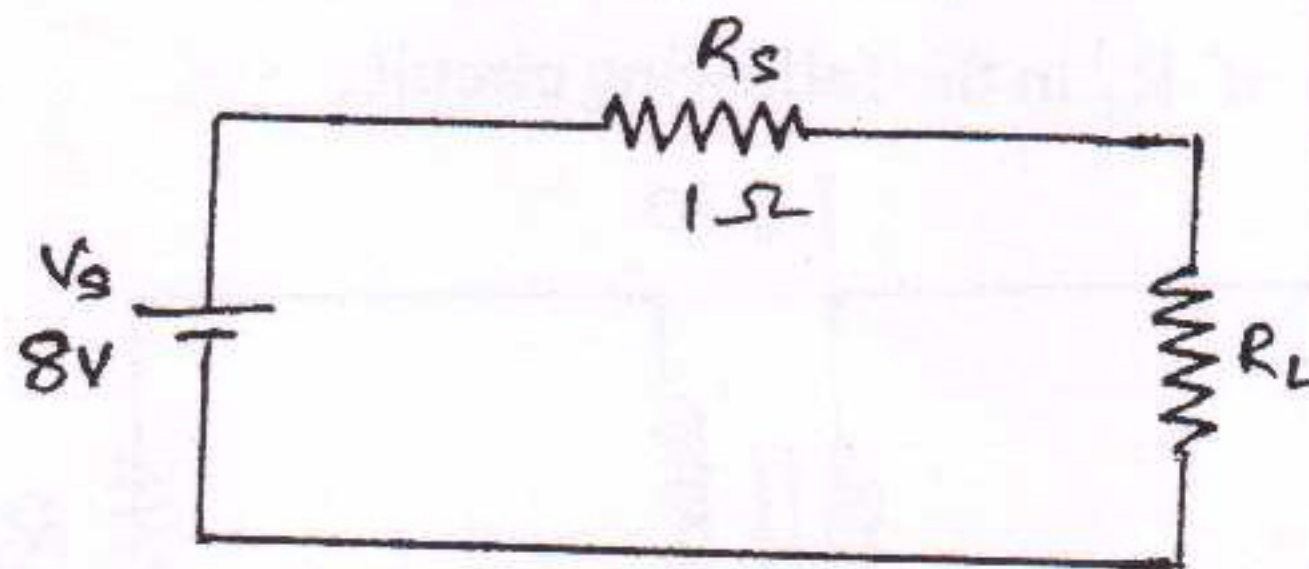- f) In the following circuit : 1) What is  $I_L$  when  $R_L = 0$  ?  
2) What is  $V_L$  when  $R_L = \infty$  ?



- g) Determine  $V_0$  and  $I_D$  in the following circuit.

